 




Computer Architecture & Microprocessor System

SEQUENTIAL LOGIC DESIGN

Dennis A. N. Gookyi





CONTENTS


❖ Sequential Logic Design





BIG PICTURE: BUILDING A PROCESSOR


❖ Single cycle processor

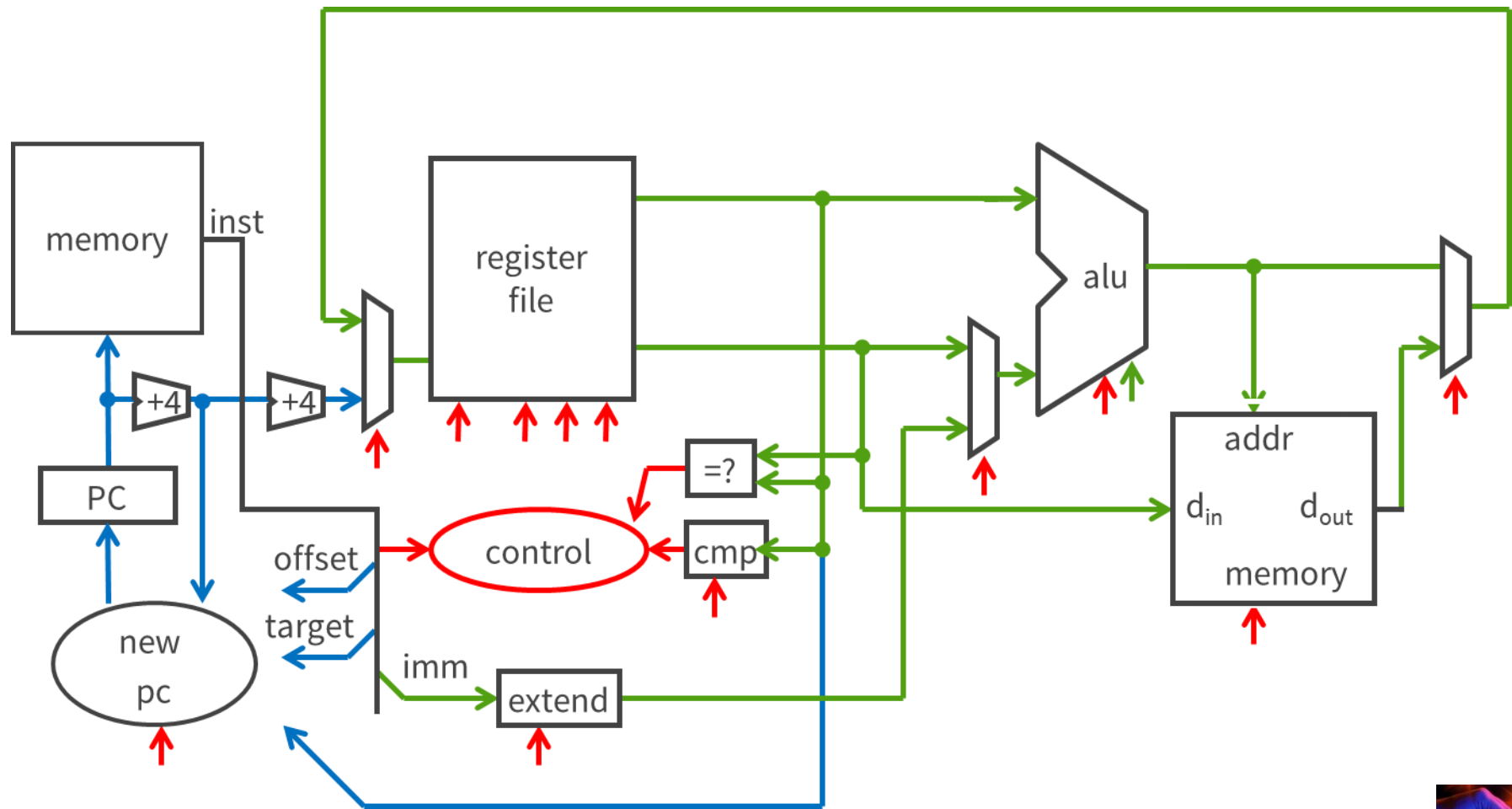



INTRODUCTION

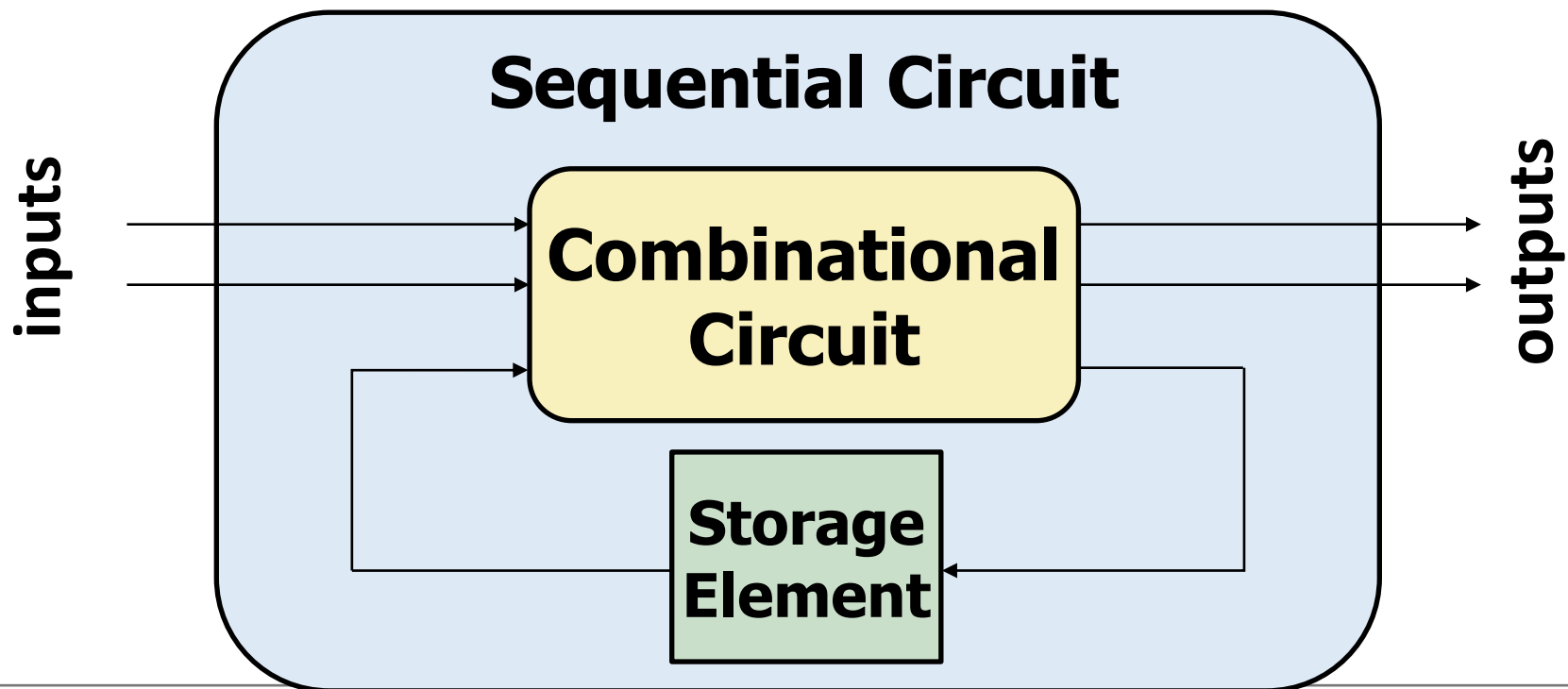- ❖ Combinational circuit output depends **only** on **current** input
- ❖ We want circuits that produce output depending on **current** and **past** input values – circuits with **memory**
- ❖ How can we design a circuit that **stores information**?





SEQUENTIAL LOGIC CIRCUITS

- ❖ We have examined designs of circuit elements that can store information
- ❖ Now, we will use these elements to build circuits that remember past inputs



Combinational

Only depends on current inputs



Sequential

Opens depending on past inputs






STATE

- ❖ In order for this lock to work, it has to keep track (**remember**) of the past events!
- ❖ If passcode is R13-L22-R3, sequence of **states** to unlock:
 - A. The lock is not open (locked), and no relevant operations have been performed
 - B. Locked but user has completed R13
 - C. Locked but user has completed R13-L22
 - D. Unlocked: user has completed R13-L22-R3
- ❖ The **state** of a system is a snapshot of all relevant elements of the system at the moment of the snapshot
 - To open the lock, **states A-D must be completed in order**
 - If anything else happens (e.g., L5), lock **returns** to state A



STATE DIAGRAM

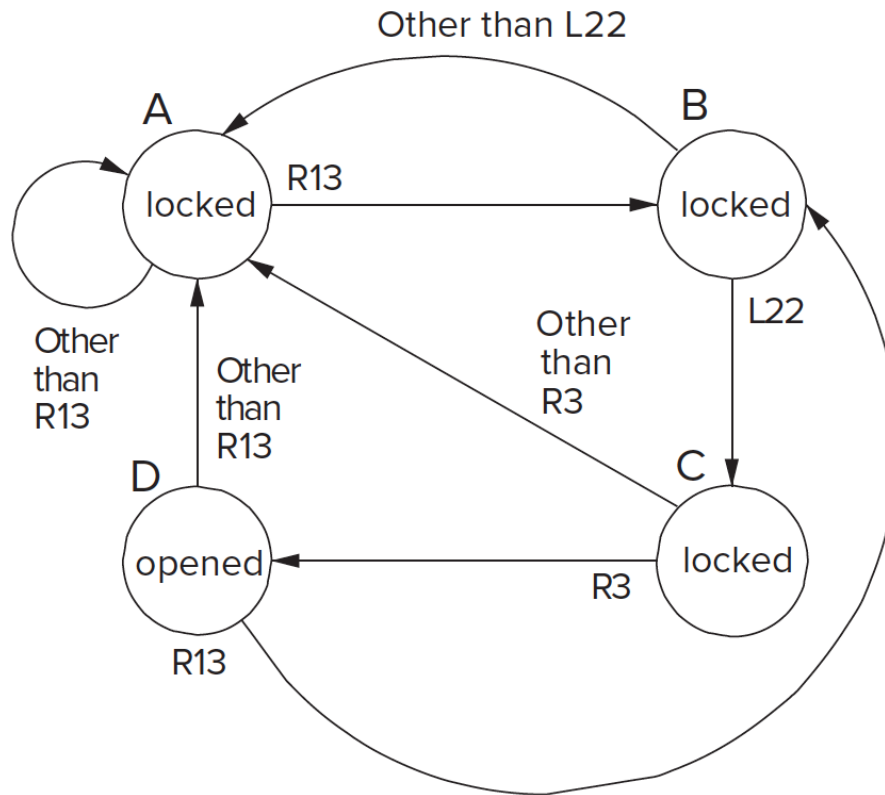- ❖ Completely describes the operation of the sequential lock



- ❖ We will understand "state diagrams" fully later today





STATE DIAGRAM

❖ Asynchronous vs. Synchronous State Changes

- Sequential lock we saw is an asynchronous “machine”
 - State transitions occur when they occur
 - There is nothing that synchronizes when each state transition must occur
- Most modern computers are synchronous “machines”
 - State transitions take place after fixed units of time
 - Controlled in part by a clock, as we will see soon
- These are two different design paradigms, with tradeoffs







STATE DIAGRAM

❖ A standard Swiss traffic light has 4 states

 - A. Green
- B. Yellow
- C. Red
- D. Red and Yellow




 ❖ The sequence of these states are always as follows





STATE DIAGRAM - CLOCK

 

- ❖ When should the light change from one state to another?
- ❖ We need a **clock** to dictate when to change state
 - Clock signal alternates between 0 & 1


 


Figure 3.28 A clock signal.

 



STATE DIAGRAM - CLOCK



- ❖ When should the light change from one state to another?
- ❖ We need a **clock** to dictate when to change state

- ☐ Clock signal alternates between 0 & 1



- ❖ At the start of a clock cycle (), system state changes
 - ☐ During a clock cycle, the state stays constant
 - ☐ In this traffic light example, we are assuming the traffic light stays in each state an equal amount of time





STATE DIAGRAM - CLOCK

- ❖ Clock is a general mechanism that triggers transition from one state to another in a (synchronous) sequential circuit
- ❖ Clock synchronizes state changes across many sequential circuit elements
- ❖ Combinational logic evaluates for the length of the clock cycle
- ❖ Clock cycle should be chosen to accommodate maximum combinational circuit delay





STATE DIAGRAM

❖ Asynchronous vs. Synchronous State Changes

- Sequential lock we saw is an asynchronous “machine”
 - State transitions occur when they occur
 - There is nothing that synchronizes when each state transition must occur
- Most modern computers are synchronous “machines”
 - State transitions take place after fixed units of time
 - Controlled in part by a clock, as we will see soon
- These are two different design paradigms, with tradeoffs
 - Synchronous control can be easier to get correct when the system consists of many components and many states
 - Asynchronous control can be more efficient (no clock overheads)





FINITE STATE MACHINE (FSM)

- ❖ What is a Finite State Machine (FSM)?
 - A discrete-time model of a stateful system
 - Each state represents a snapshot of the system at a given time

- ❖ An FSM pictorially shows
 - The set of all possible states that a system can be in
 - How the system transitions from one state to another

- ❖ An FSM can model
 - A traffic light, an elevator, fan speed, a microprocessor, etc.

- ❖ An FSM enables us to pictorially think of a stateful system using simple diagrams





FINITE STATE MACHINE (FSM)

❖ FSM consist of five elements:

- A finite number of states
 - State: snapshot of all relevant elements of the system at the time of the snapshot
- A finite number of external inputs
- A finite number of external outputs
- An explicit specification of all state transitions
 - How to get from one state to another
- An explicit specification of what determines each external output value






FINITE STATE MACHINE (FSM)

❖ Each FSM consists of three separate parts:

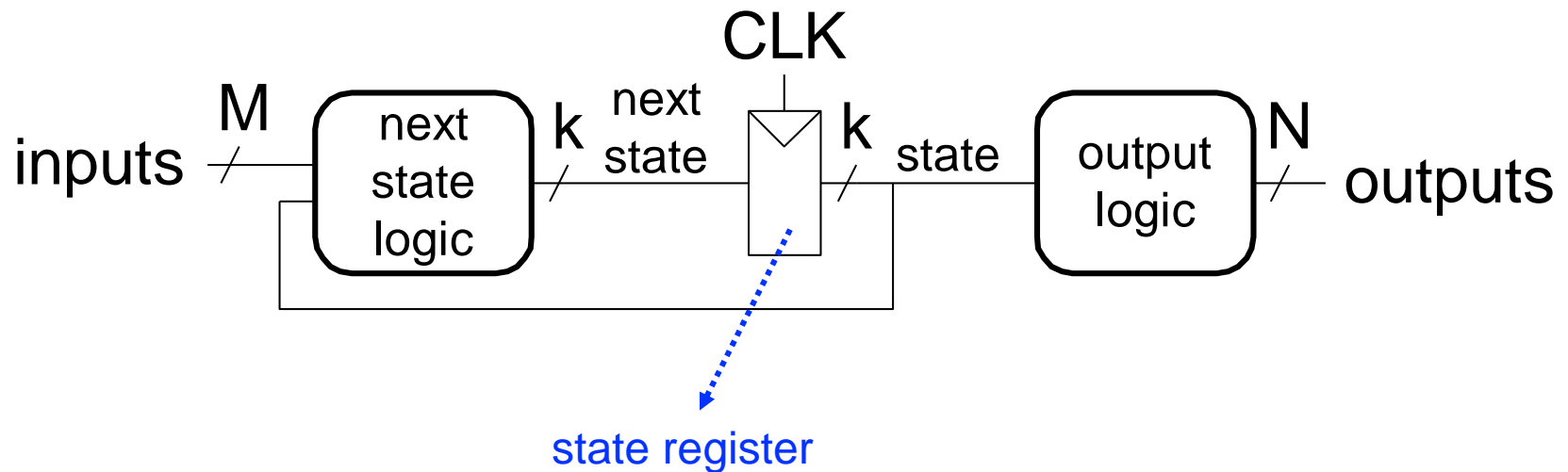- next state logic
- state register
- output logic



At the beginning of the clock cycle, next state is latched into the state register






FINITE STATE MACHINE (FSM)



❖ Sequential Circuits

 - State register(s)
 - Store the current state and
 - Load the next state at the clock edge



❖ Combinational Circuits

  - Next state logic
 - Determines what the next state will be
- Output logic
 - Generates the outputs







FINITE STATE MACHINE (FSM)

- ❖ Next state is determined by the current state and the inputs
- ❖ Two types of finite state machines differ in the output logic:
 - Moore FSM: outputs depend only on the current state
 - Mealy FSM: outputs depend on the current state and the inputs

Moore FSM

 

Mealy FSM

 



FINITE STATE MACHINE (FSM)

❖ Example: “Smart” traffic light controller

□ 2 inputs:


- Traffic sensors: T_A , T_B (TRUE when there's traffic)

□ 2 outputs:

- Lights: L_A , L_B (Red, Yellow, Green)

□ State can change every 5 seconds

 
- Except if green and traffic, stay green





FINITE STATE MACHINE (FSM)

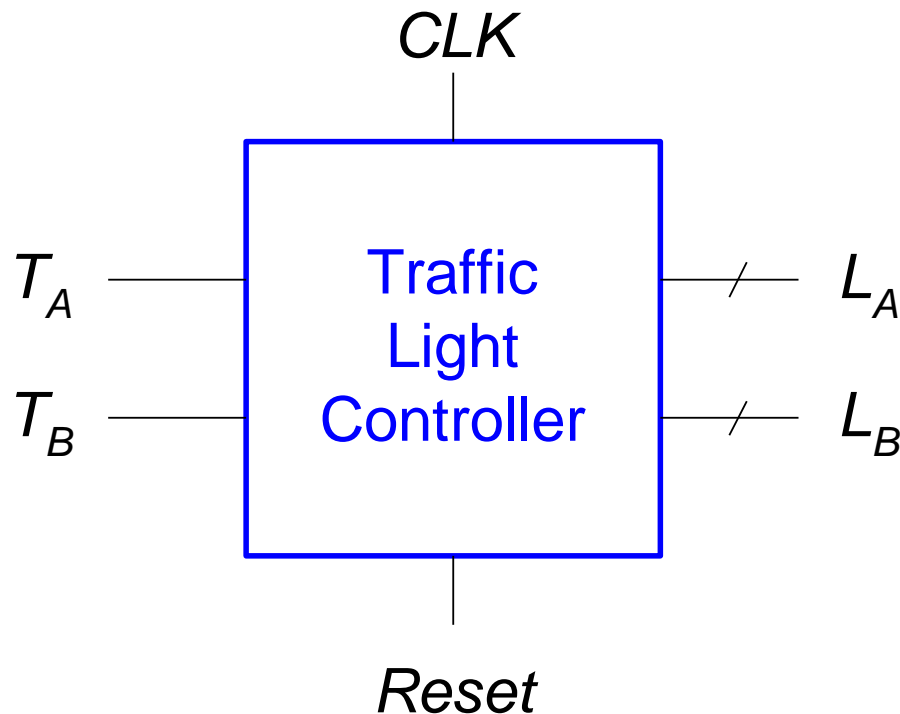- ❖ Inputs: CLK, Reset, T_A , T_B
- ❖ Outputs: L_A , L_B







FINITE STATE MACHINE (FSM)

❖ Moore FSM: outputs labeled in each state

- States: Circles
- Transitions: Arcs

 
 




FINITE STATE MACHINE (FSM)

❖ Moore FSM: outputs labeled in each state

- States: Circles
- Transitions: Arcs

 
 




FINITE STATE MACHINE (FSM)

❖ Moore FSM: outputs labeled in each state

- States: Circles
- Transitions: Arcs

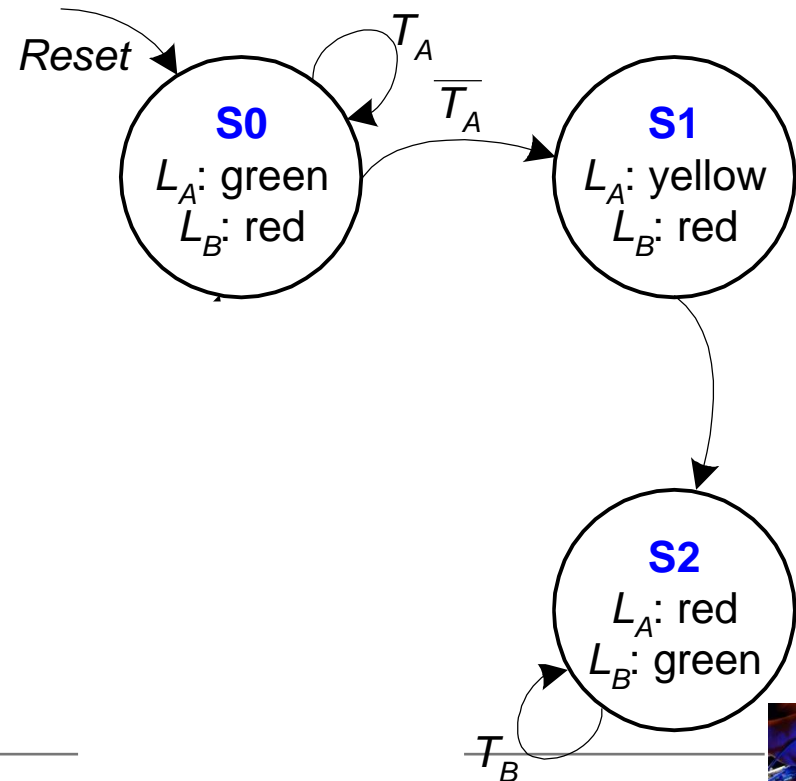
 




FINITE STATE MACHINE (FSM)

❖ Moore FSM: outputs labeled in each state

- States: Circles
- Transitions: Arcs

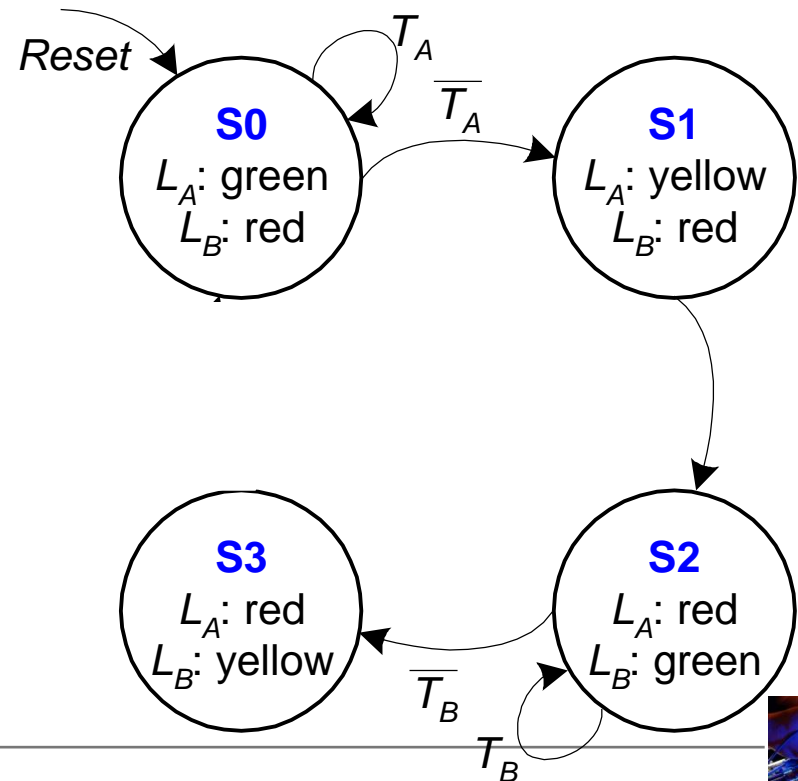
 




FINITE STATE MACHINE (FSM)

❖ Moore FSM: outputs labeled in each state


- States: Circles
- Transitions: Arcs

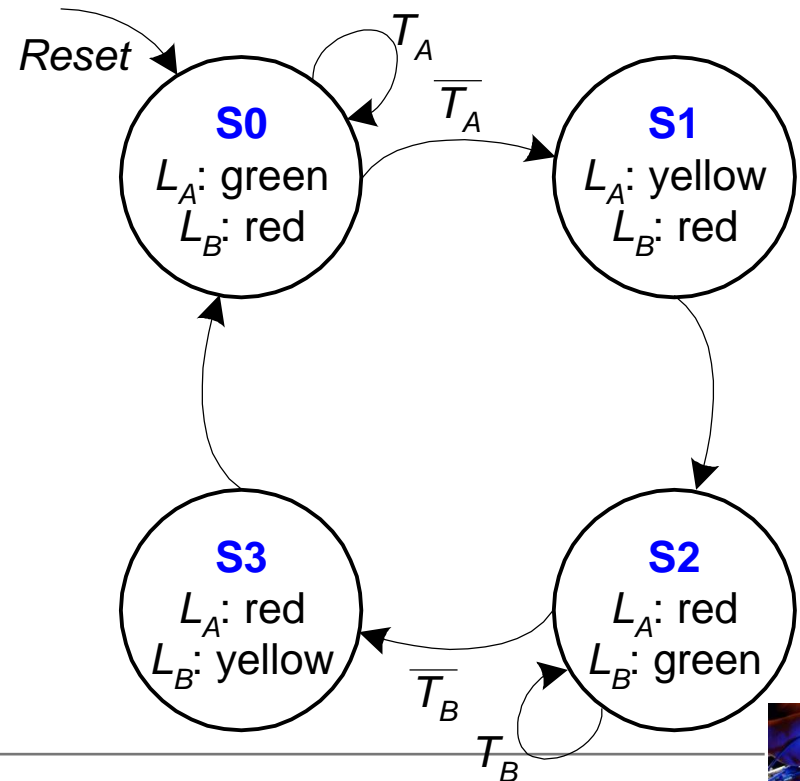 



FSM – STATE TRANSITION TABLE

❖ State transition table

 


Current State	Inputs		Next State
S	T_A	T_B	S'
S0	0	X	
S0	1	X	
S1	X	X	
S2	X	0	
S2	X	1	
S3	X	X	



FSM – STATE TRANSITION TABLE

❖ State transition table

 


Current State	Inputs		Next State
S	T_A	T_B	S'
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0



FSM – STATE TRANSITION TABLE

❖ State transition table

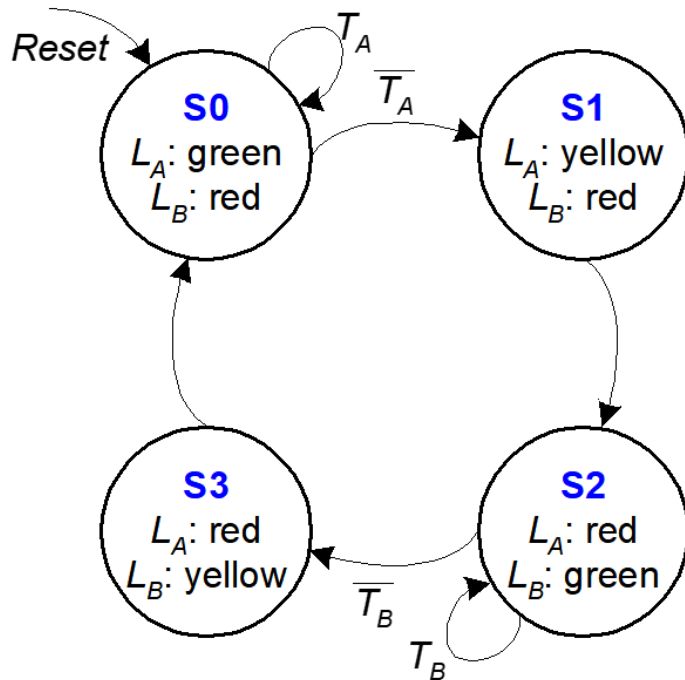


Current State	Inputs		Next State
S	T_A	T_B	S'
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0

State	Encoding
S0	00
S1	01
S2	10
S3	11

FSM – STATE TRANSITION TABLE

❖ State transition table

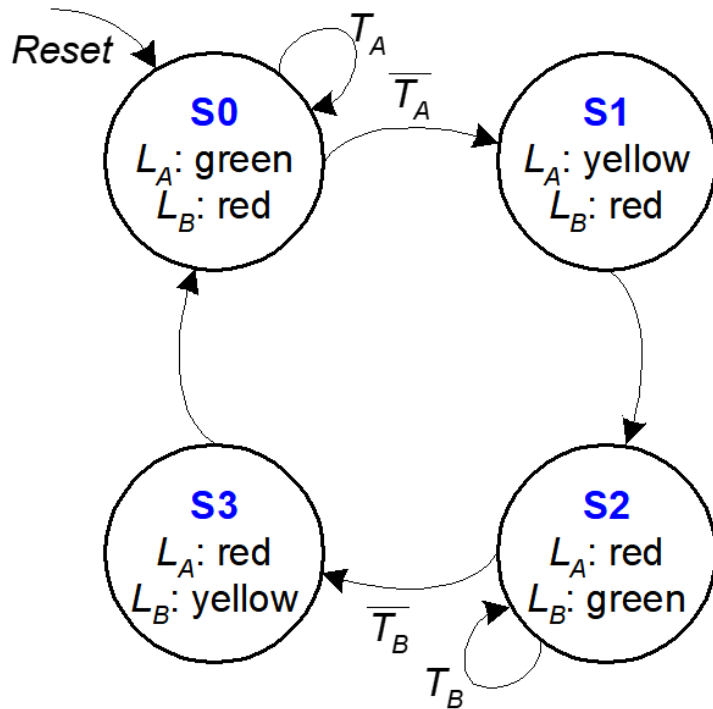


Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

FSM – STATE TRANSITION TABLE

❖ State transition table

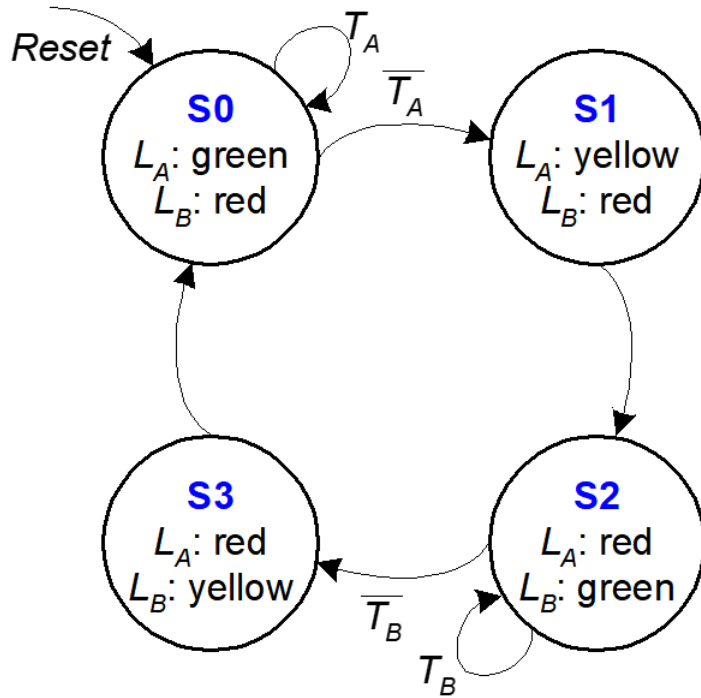


$S'_1 = ?$

Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

FSM – STATE TRANSITION TABLE

❖ State transition table

 


Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = (\bar{S}_1 \cdot S_0) + (S_1 \cdot \bar{S}_0 \cdot \bar{T}_B) + (S_1 \cdot \bar{S}_0 \cdot T_B)$$

FSM – STATE TRANSITION TABLE

❖ State transition table

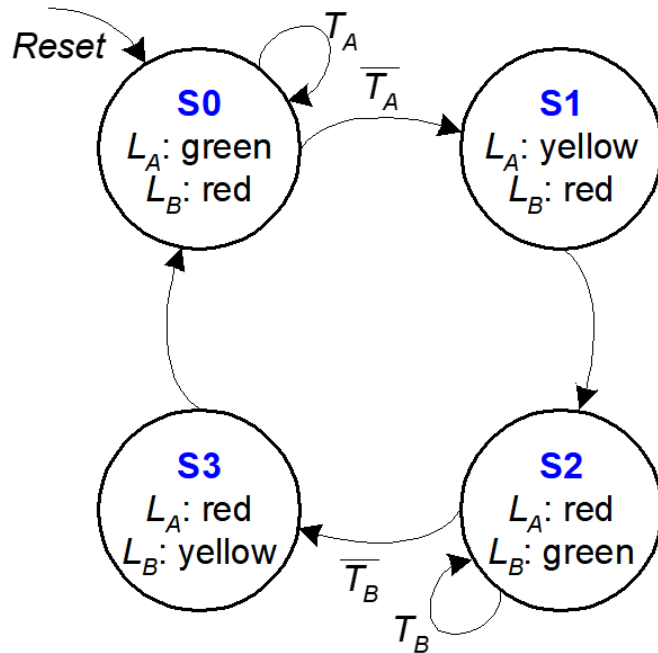

Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11


$$S'_1 = (\overline{S_1} \cdot S_0) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B}) + (S_1 \cdot \overline{S_0} \cdot T_B)$$

$$S'_0 = ?$$



FSM – STATE TRANSITION TABLE

❖ State transition table

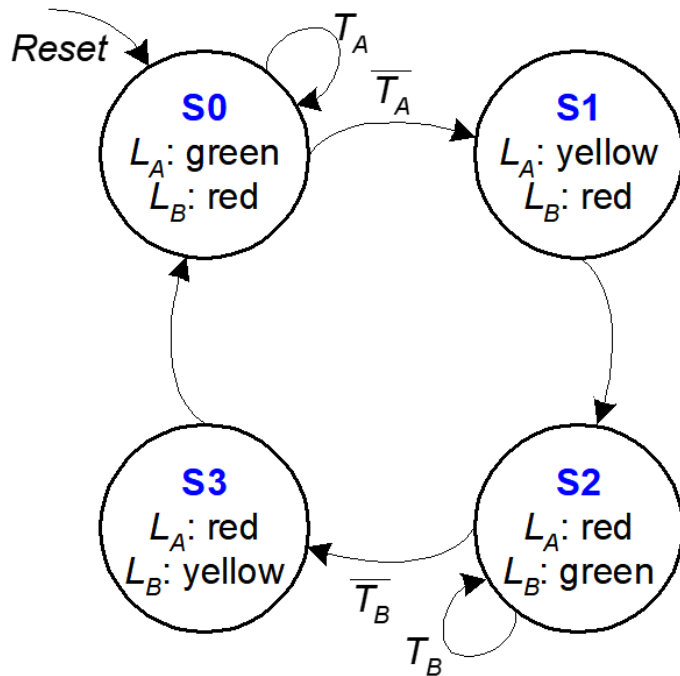

Current State		Inputs		Next State	
S ₁	S ₀	T _A	T _B	S' ₁	S' ₀
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0


State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = (\bar{S}_1 \cdot S_0) + (S_1 \cdot \bar{S}_0 \cdot \bar{T}_B) + (S_1 \cdot \bar{S}_0 \cdot T_B)$$

$$S'_0 = (\bar{S}_1 \cdot \bar{S}_0 \cdot \bar{T}_A) + (S_1 \cdot \bar{S}_0 \cdot \bar{T}_B)$$

FSM – STATE TRANSITION TABLE

❖ State transition table

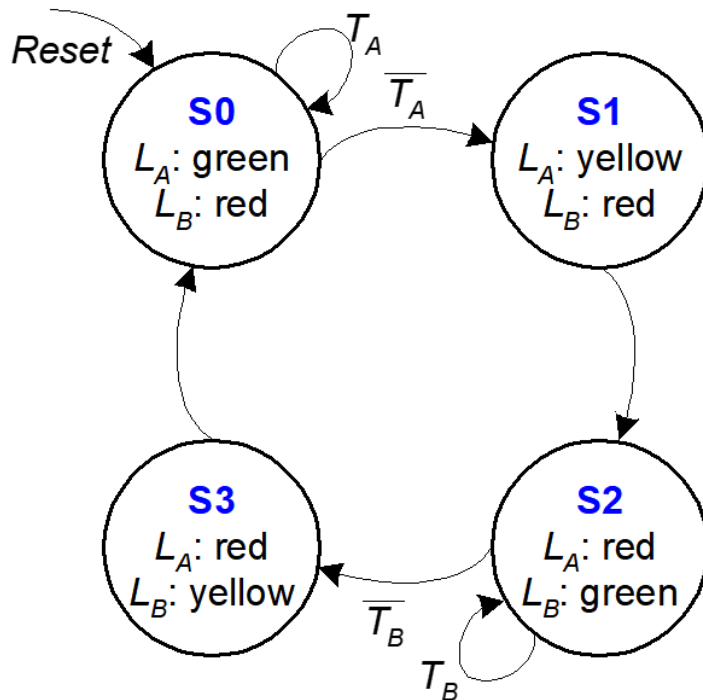

Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11


$$S'_1 = S_1 \text{ xor } S_0 \quad \textbf{(Simplified)}$$

$$S'_0 = (\bar{S}_1 \cdot \bar{S}_0 \cdot \bar{T}_A) + (S_1 \cdot \bar{S}_0 \cdot \bar{T}_B)$$



FSM – OUTPUT TABLE

❖ Output table

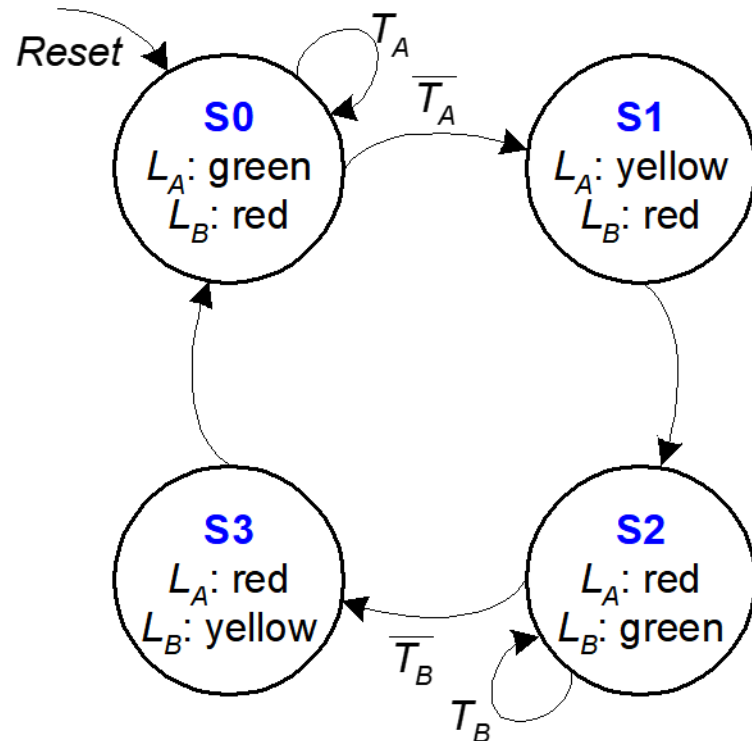


Current State		Outputs	
S_1	S_0	L_A	L_B
0	0	green	red
0	1	yellow	red
1	0	red	green
1	1	red	yellow



FSM – OUTPUT TABLE

❖ Output table

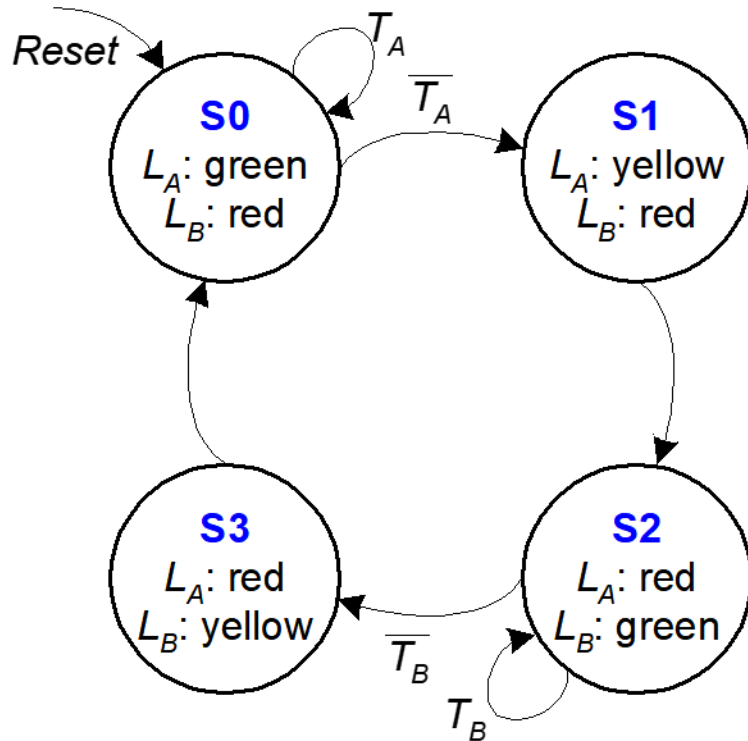


Current State		Outputs	
S_1	S_0	L_A	L_B
0	0	green	red
0	1	yellow	red
1	0	red	green
1	1	red	yellow

Output	Encoding
green	00
yellow	01
red	10

FSM – OUTPUT TABLE

❖ Output table

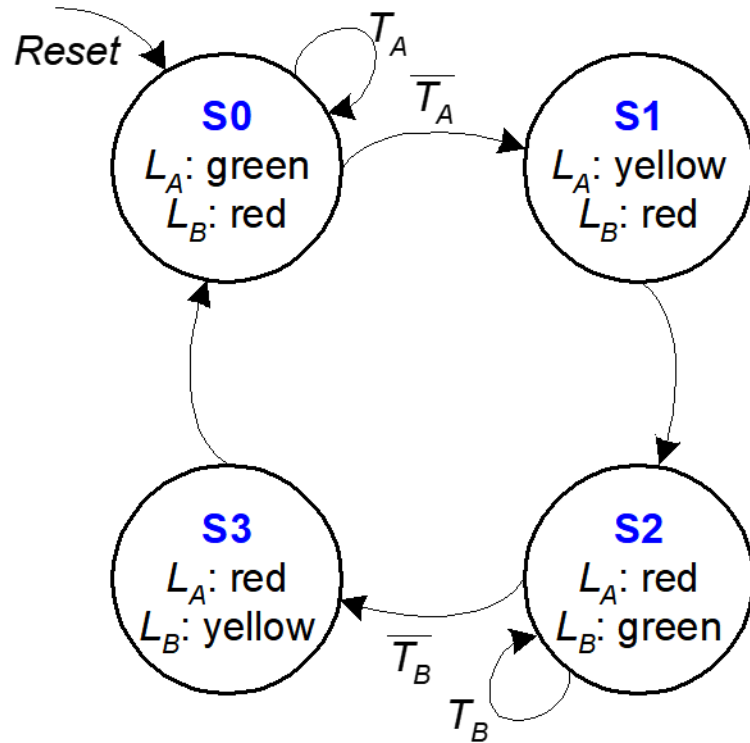


Current State		Outputs			
S_1	S_0	L_{A1}	L_{A0}	L_{B1}	L_{B0}
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10

FSM – OUTPUT TABLE

❖ Output table

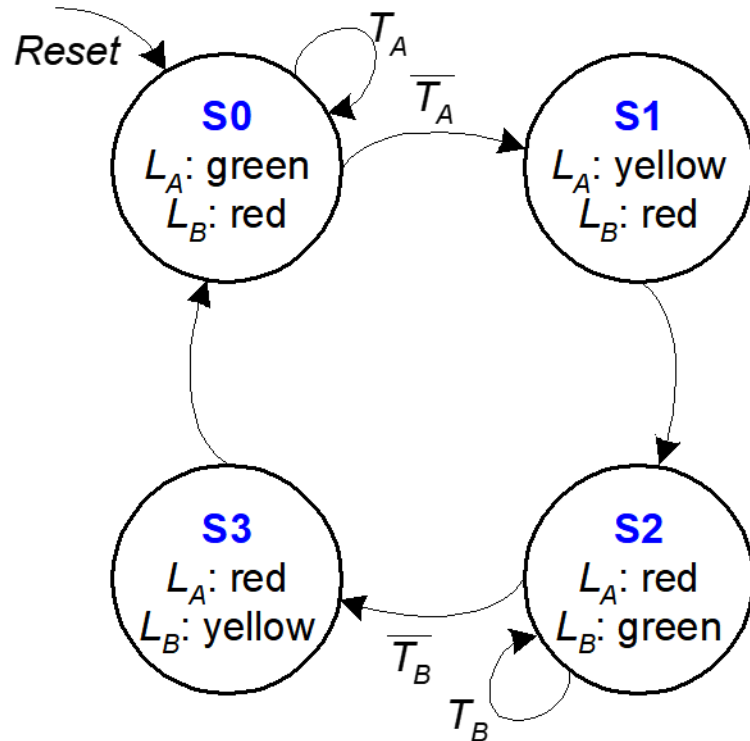

$$L_{A1} = S_1$$


$$L_{A0} = \overline{S_1} \cdot S_0$$

Current State		Outputs			
S_1	S_0	L_{A1}	L_{A0}	L_{B1}	L_{B0}
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10

FSM – OUTPUT TABLE

❖ Output table

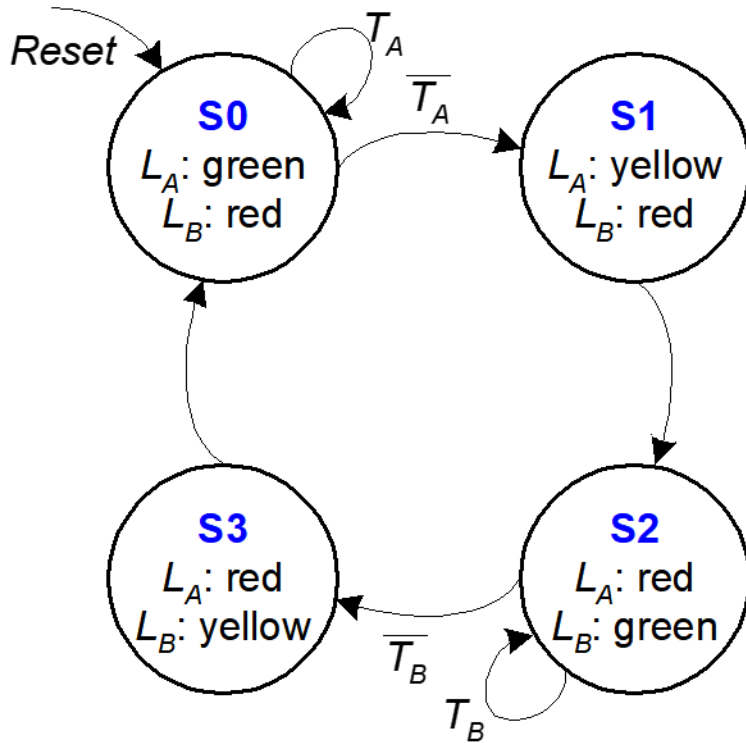


Current State		Outputs			
S_1	S_0	L_{A1}	L_{A0}	L_{B1}	L_{B0}
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10

$$\begin{aligned}
 L_{A1} &= S_1 \\
 L_{A0} &= \overline{S_1} \cdot S_0 \\
 L_{B1} &= \overline{S_1}
 \end{aligned}$$

FSM – OUTPUT TABLE

❖ Output table

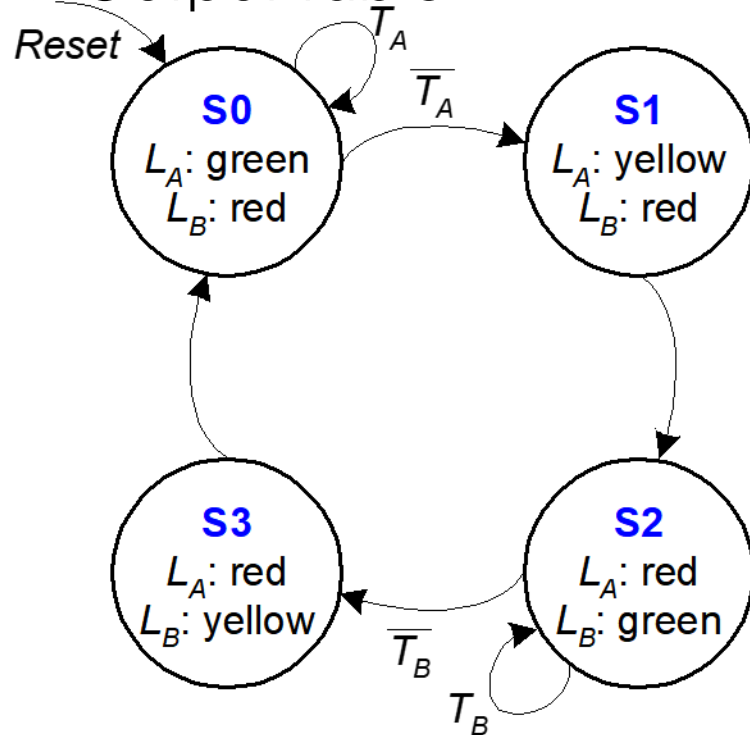

Current State		Outputs			
S_1	S_0	L_{A1}	L_{A0}	L_{B1}	L_{B0}
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10

$$L_{A1} = \overline{S_1}$$

$$L_{A0} = \overline{S_1} \cdot S_0$$


$$L_{B1} = \overline{S_1}$$

$$L_{B0} = S_1 \cdot S_0$$



FSM – SCHEMATIC


❖ Overview

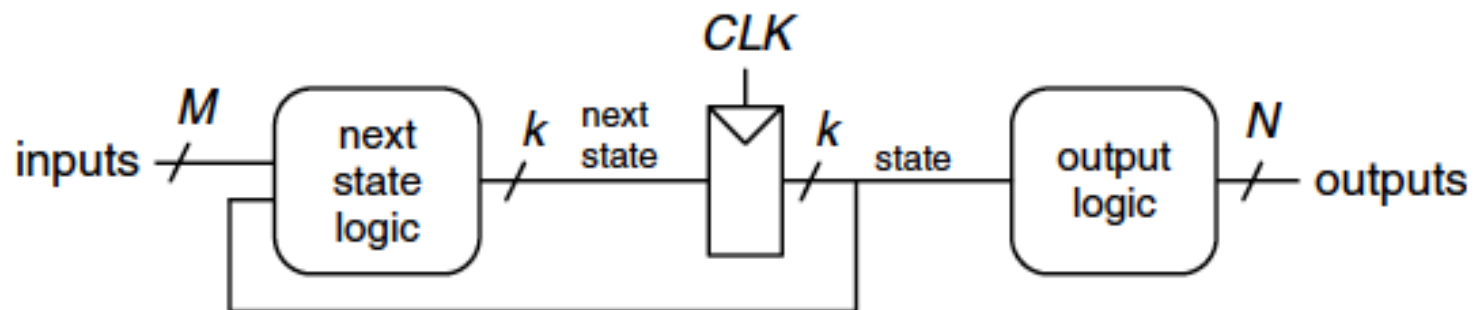



FSM – SCHEMATIC


❖ State register

 



FSM – SCHEMATIC

❖ Next state logic

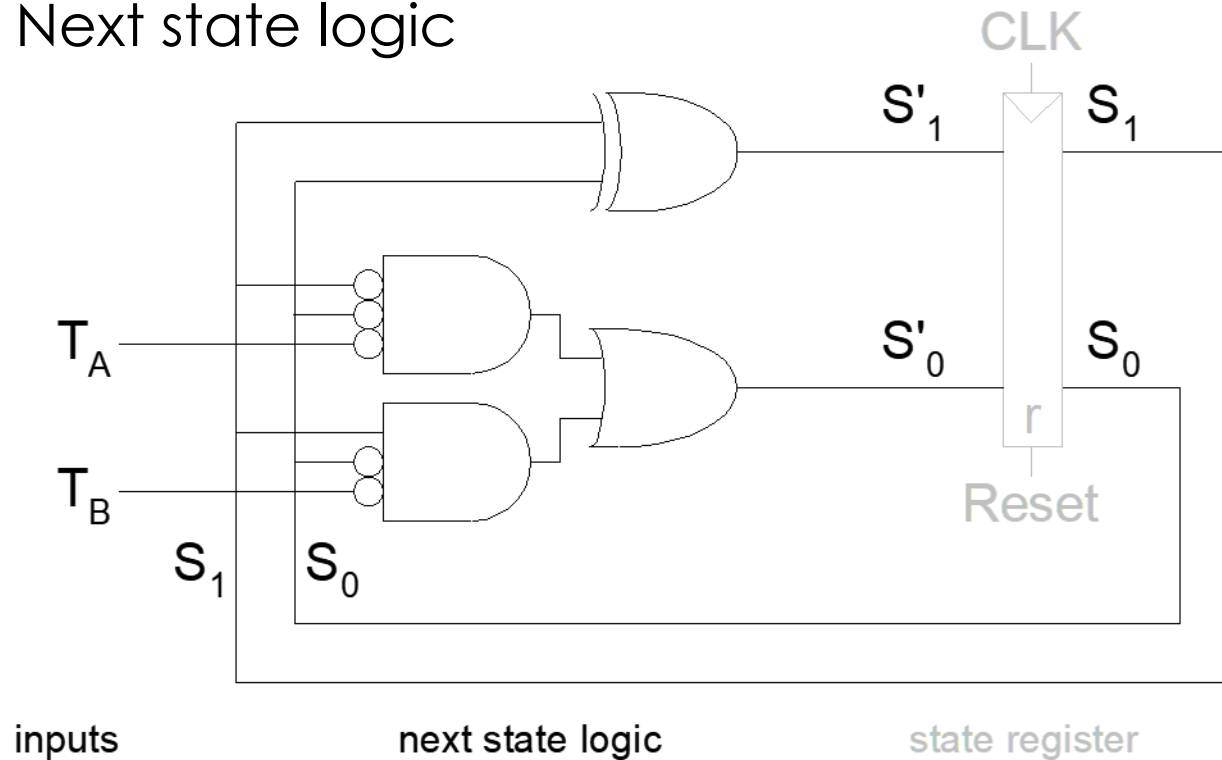

$$S'_1 = S_1 \text{ xor } S_0$$


$$S'_0 = (\overline{S_1} \cdot \overline{S_0} \cdot \overline{T_A}) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B})$$





FSM – SCHEMATIC

❖ Output logic

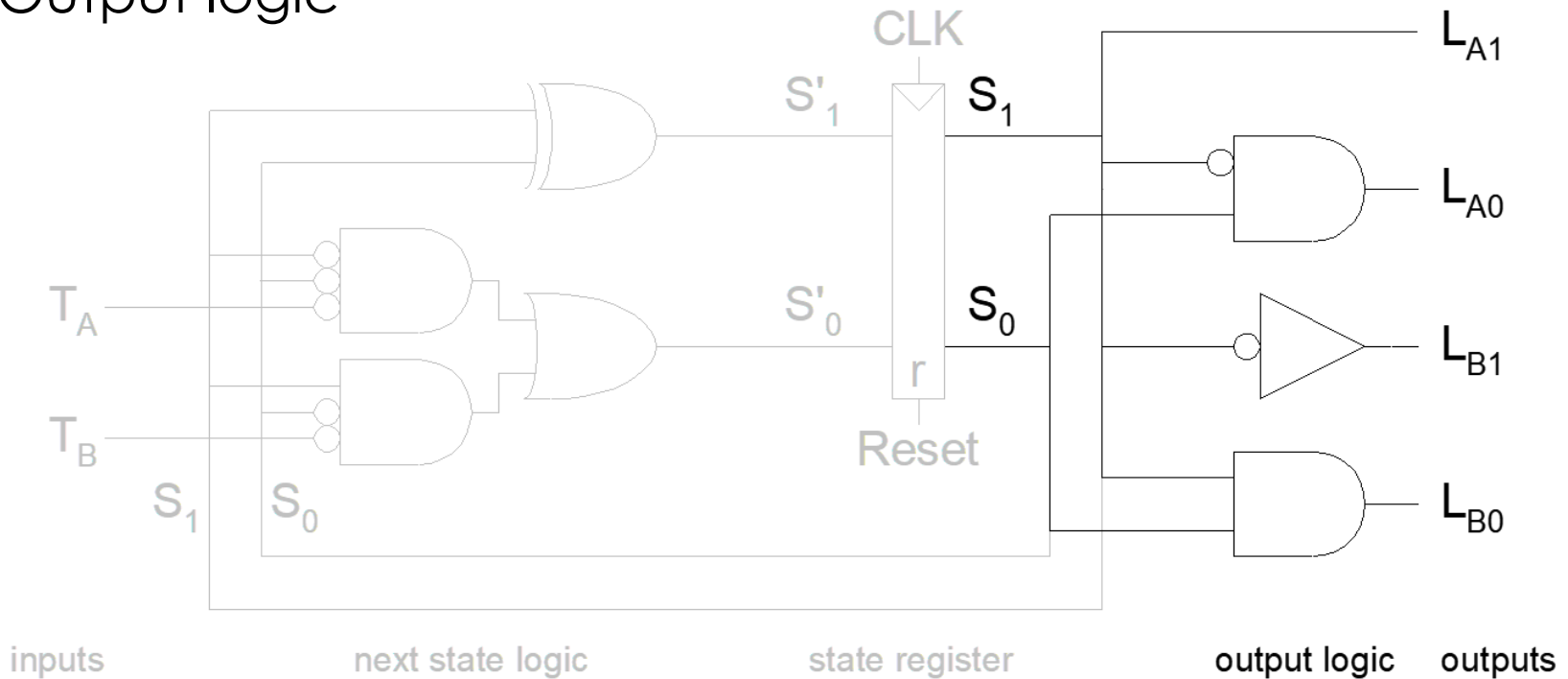


$$\begin{aligned} L_{A1} &= \overline{S_1} \\ L_{A0} &= \overline{S_1} \cdot S_0 \\ L_{B1} &= \overline{S_1} \\ L_{B0} &= S_1 \cdot S_0 \end{aligned}$$





FSM – TIMING DIAGRAM

❖ Timing diagram

 



CLK_
 Reset_
 T_A_
 T_B_
 S'_{1:0}_
 S_{1:0}_
 L_{A1:0}_
 L_{B1:0}_





FSM – TIMING DIAGRAM



❖ Timing diagram

  



FSM – TIMING DIAGRAM



❖ Timing diagram

  



FSM – TIMING DIAGRAM



❖ Timing diagram

  



FSM – TIMING DIAGRAM



❖ Timing diagram

  



FSM – TIMING DIAGRAM



❖ Timing diagram

  



FSM – TIMING DIAGRAM



❖ Timing diagram

  



FSM – TIMING DIAGRAM



❖ Timing diagram

  



FSM – TIMING DIAGRAM



❖ Timing diagram

  



FSM – TIMING DIAGRAM


❖ Timing diagram

  



FSM – STATE ENCODING

 - ❖ How do we encode the state bits?
- ❖ Three common state binary encodings with different tradeoffs
 - ☐ Fully Encoded
 - ☐ 1-Hot Encoded
 - ☐ Output Encoded
- ❖ Let's see an example Swiss traffic light with 4 states
 - ☐ Green, Yellow, Red, Yellow+Red





FSM – STATE ENCODING

❖ Binary Encoding (Full Encoding):

- Use the minimum possible number of bits
 - Use $\log_2(\text{num_states})$ bits to represent the states
- Example state encodings: 00, 01, 10, 11
- Minimizes # flip-flops, but not necessarily output logic or next state logic





FSM – STATE ENCODING

❖ One-Hot Encoding:

- Each bit encodes a different state
 - Uses num_states bits to represent the states
 - Exactly 1 bit is “hot” for a given state
- Example state encodings: 0001, 0010, 0100, 1000
- Simplest design process – very automatable
- Maximizes # flip-flops, minimizes next state logic





FSM – STATE ENCODING

❖ Output Encoding:

- Outputs are directly accessible in the state encoding
- For example, since we have 3 outputs (light color), encode state with 3 bits, where each bit represents a color
- Example states: 001, 010, 100, 110
 - Bit0 encodes green light output,
 - Bit1 encodes yellow light output
 - Bit2 encodes red light output
- Minimizes output logic
- Only works for Moore Machines (output function of state)





FSM – STATE ENCODING

- ❖ The designer must carefully choose an encoding scheme to optimize the design under given constraints

